## **COMP 3315 Lab 9: Single Cycle SMIPS Connections**

Read specifications below carefully.

## Build:

- a) Create a PC component as 8 bit Register.
- b) Create Multiplexers with respect to given data path diagram.
- c) Create RAM with given specifications.
- **d)** Create Inputs for control signals (RegDst,Jump,ALUSrc,MemtoReg,RegWrite,MemRead,MemWrite,Branch)
- e) Use splitters to divide Instruction bit partitions.
- f) Connect the cables according to diagram.

## Test:

Provide instruction and all control signals for each of these instructions of the following MIPS program.

```
addi $1, $0, 9 # reg1 = 0x00001001
addi $2, $0, 6 # reg 2 = 0x00000110
or $3, $1, $2 # reg 3 = 0x00001111
```

You should see 0x00001111 stored in register 3 of register file if everything works.

After:

```
sw $3, 3($1) # RAM location 12 should have 0x00001111
lw $4, 3($1) # Register 4 should gave 0x00001111
```

You are expected to implement your Datapath design and Upload .circ file for your labwork. (If you import different .circ files include them)

## Specifications for SMIPS Datapath

Instruction Types:

Memory-reference: lw, sw

• Arithmetic-logical: AND, OR, Add, Sub, Slt, XOR, XNOR and NOR, addi

Control flow: beq, j

Memory Specifications:

- Instruction Memory: 256 x 8 (8-bit word addressing / 8-bit words)
  - The least significant 8 bits of Instruction is used
- Data Memory: 256 x 8 (8-bit word addressing / 8-bit words)
  - 8 bits of ALU result is used

Memory-reference instruction specifications:

- For sw and lw, an immediate value in the interval  $[-2^7, 2^7-1]$  is used as offset.
  - Memory address is the least significant 8 bits of Reg[Ins[14..12]] + Ins[7..0]

Control flow specifications:

- For beq, an immediate value in the interval [-2<sup>7</sup>, 2<sup>7</sup>-1] is used to compute the branch address.
  - Branch address is PC + 1 + Ins[7..0]
- For j, the least significant 8 bits of the instruction is used directly as the jump address.
  - Jump address is Ins[7..0]

Immediate Instruction specifications:

- addi instruction is included.
  - Reg[Ins[11..9]] = Reg[Ins[14..12]] + Ins[7..0]

